

## Resistance, Circuits, and Power

1. Complete the following sentences with words from the list below. (The words may be used more than once, and all words may not necessarily be used.)


- (a) In a series circuit the Current is the same through all resistors.
- (b) The voltage is the same across resistors that are connect in parallel.
- (c) The rate at which energy is transferred is known as power.
- (d) When two batteries are connected in parallel their voltage adds together.
- (e) The energy of moving charges is transformed into heat due to resistance in a wire.

Current	Power	Series
Parallel	Resistance	Voltage

2. In an electrical circuit, if the current increases while the resistance is constant, the voltage

- (A) increases.
- (B) decreases.
- (C) remains constant.


3. Consider the following circuit.

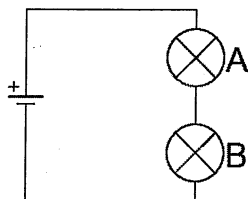

If bulb A is removed, bulb B will


- (A) get brighter.
- (B) get dimmer.
- (C) glow just as brightly as before.
- (D) go out.

4. Consider the following circuit.

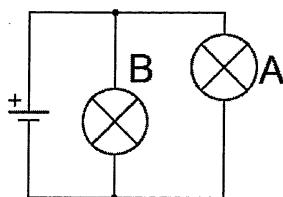


If bulb A is removed, bulb B will

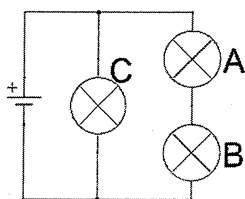- (A) get brighter.
  - (B) get dimmer.
  - ☒ (C) glow just as brightly as before.
  - (D) go out.
5. Consider the following circuit.




If bulb A is removed, bulb C will

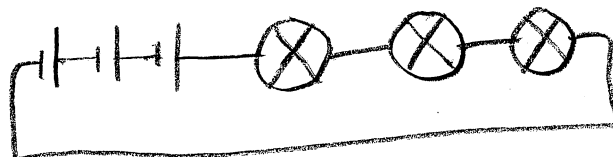
- (A) get brighter.
  - (B) get dimmer.
  - ☒ (C) glow just as brightly as before.
  - (D) go out.
5. Draw a circuit diagram for a circuit containing three batteries (cells) in series, connected to three light bulbs in series.



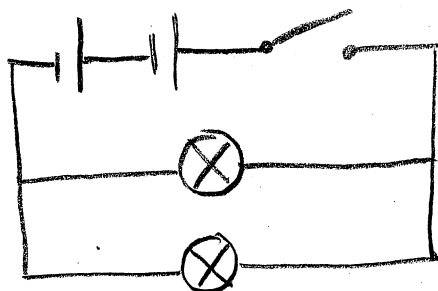6. Draw a circuit diagram of a circuit containing two batteries (cells) in series connected to two light bulbs in parallel, and a switch that controls both light bulbs at the same time.



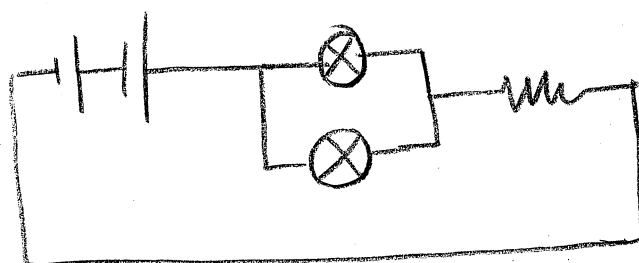7. Draw a circuit diagram of a circuit containing two batteries (cells) in series connected to two light bulbs in parallel and a resistor in series.



8. Why are the circuits in a house wired in parallel?

- All appliances receive the same amount of energy (voltage)

9. What is the purpose of a circuit breaker?

- To limit the amount of current flowing through the circuit

10. A car engine heater, rated at 750 W, is used for 8 hours each night. The cost is 9¢/kwh.

(a) Calculate the cost for

(i) 1 night.

$$\frac{750W}{1000} \times 8 \times \$0.09 = \$0.54$$

(ii) 1 month (30 days).

$$\$0.54 \times 30 = \$16.20$$

(b) How much could you save each month if the heater is used only 4 hours each night?

4 hours is half the time so

$$\frac{\$16.20}{2} = \$8.10$$

11. An electric hot water heater, rated at 1500 W, is used for 5 hours a day, 20 days a month. Electricity costs \$0.09/kWh. Calculate the monthly cost of using the hot water heater.

$$\frac{1500}{1000} \times 5 \times 20 \times \$0.09 = \$13.50$$